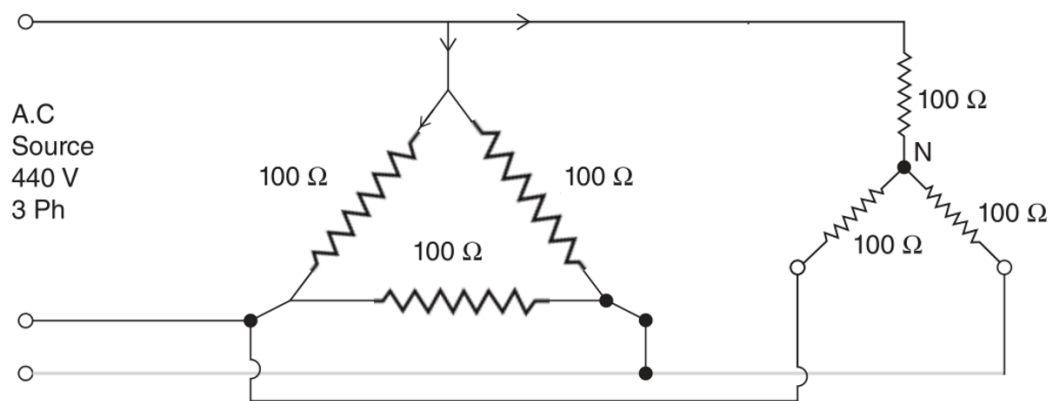


Exercises 2 (AC circuit 3-phase system)

1. A balanced ABC sequence, Y-connected source with $V_{an} = 100\angle 10^\circ$ is connected to a Δ -connected, balanced load $8+j4\Omega$ per phase. Calculate the phase and line currents of the load?
2. Three resistances, each of 100Ω , are connected in star to a three- phase 440V supply. Three resistances 100Ω connected in delta are also connected to the supply. Calculate the line current the system?



3. A 3-phase star connected system has 4Ω resistance in series with an inductance of 10mH per phase is applied voltage is 415 V (line-to-line) with 50 Hz . Find the power drawn by the circuit?