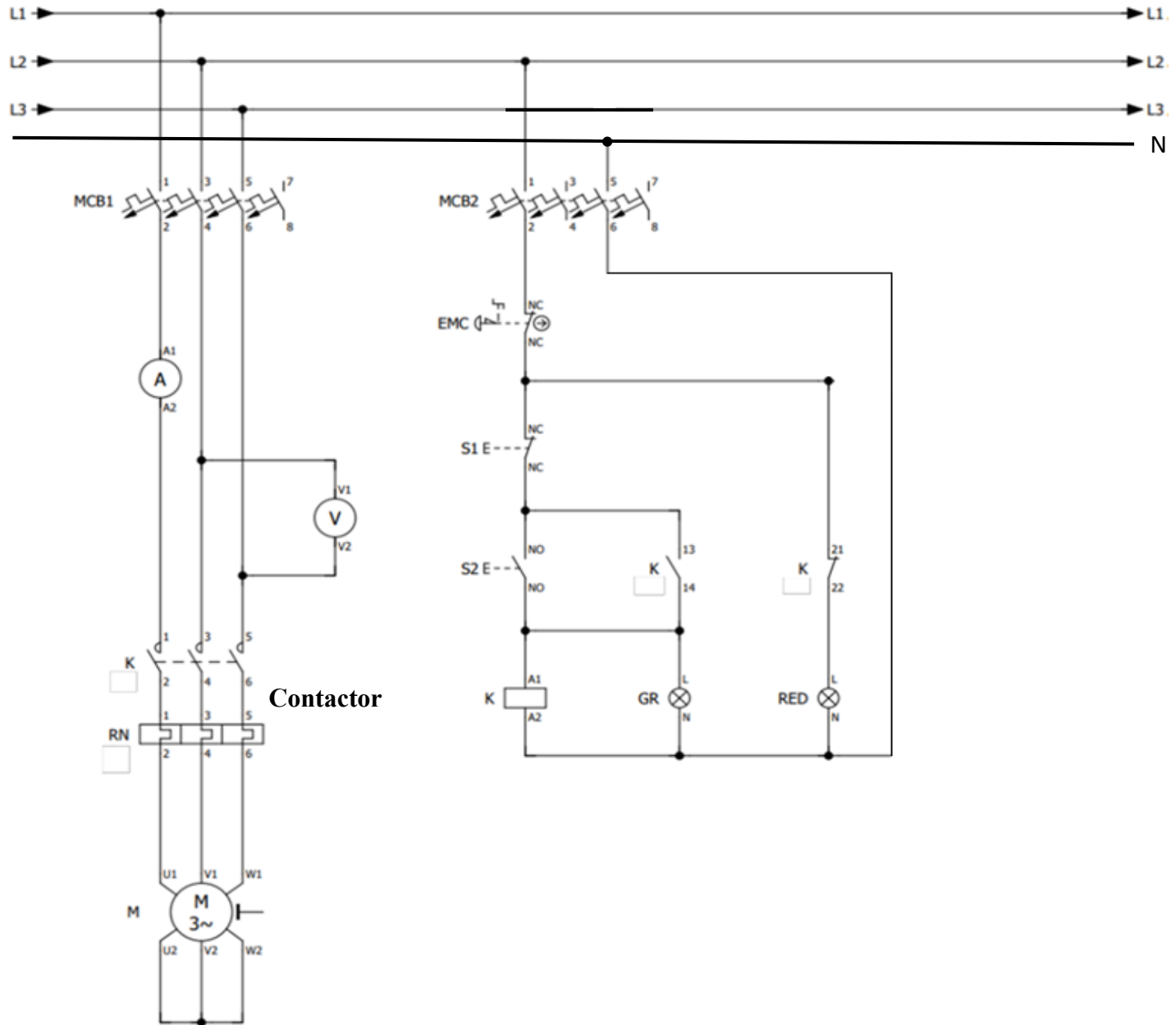


PRACTICE I

Wiring the motor as star (Y) connection in the following figure:



PRACTICE 2

Wiring two motors as star (Y) connection in the following figure:

